

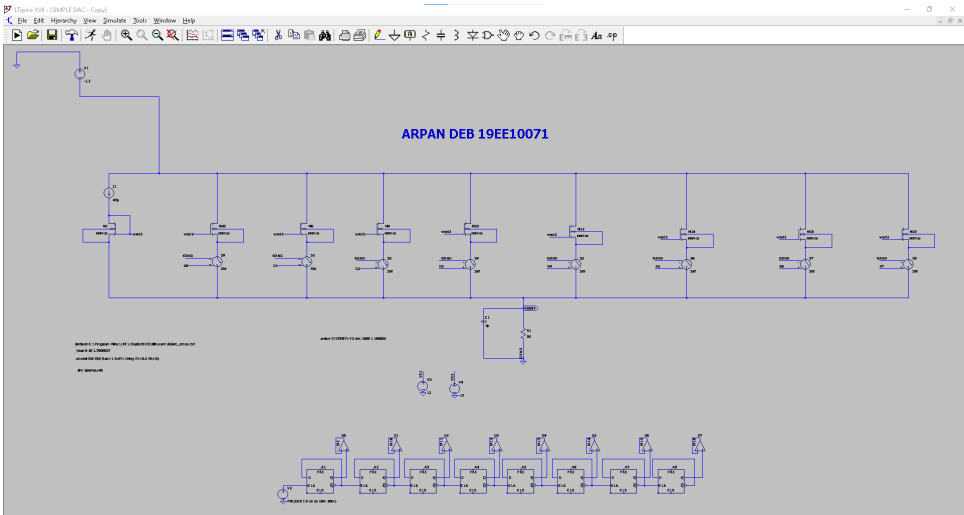



SIMPLE CURRENT MIRROR DAC

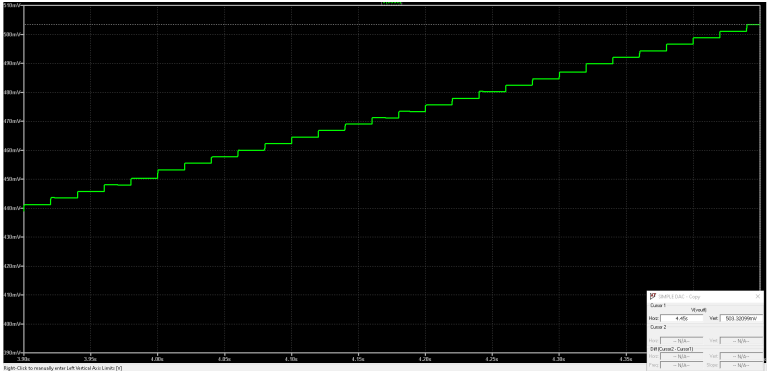


OUTPUT WAVEFORM

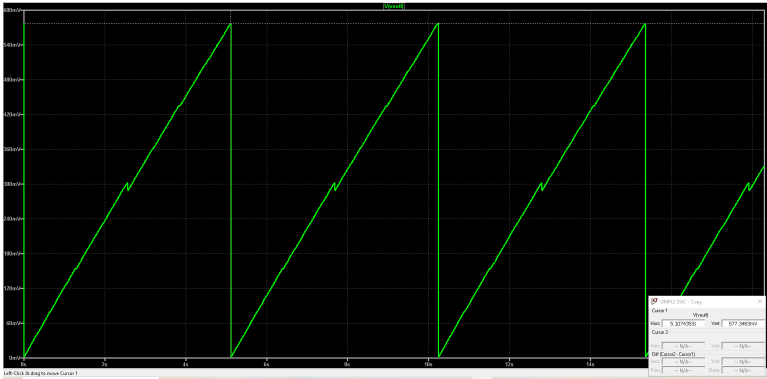


NOISE ANALYSIS

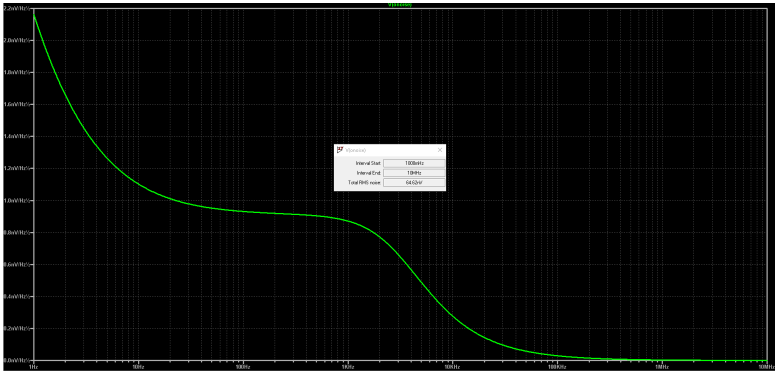


CASCODE CURRENT MIRROR DAC

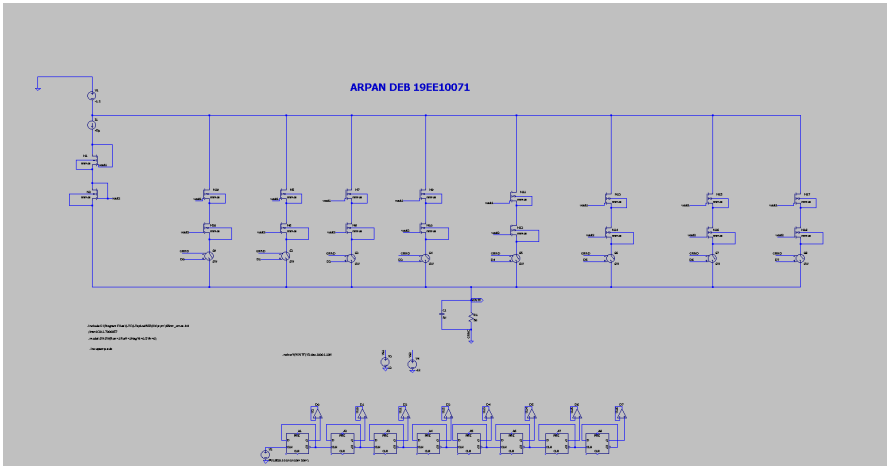


OUTPUT WAVEFORM

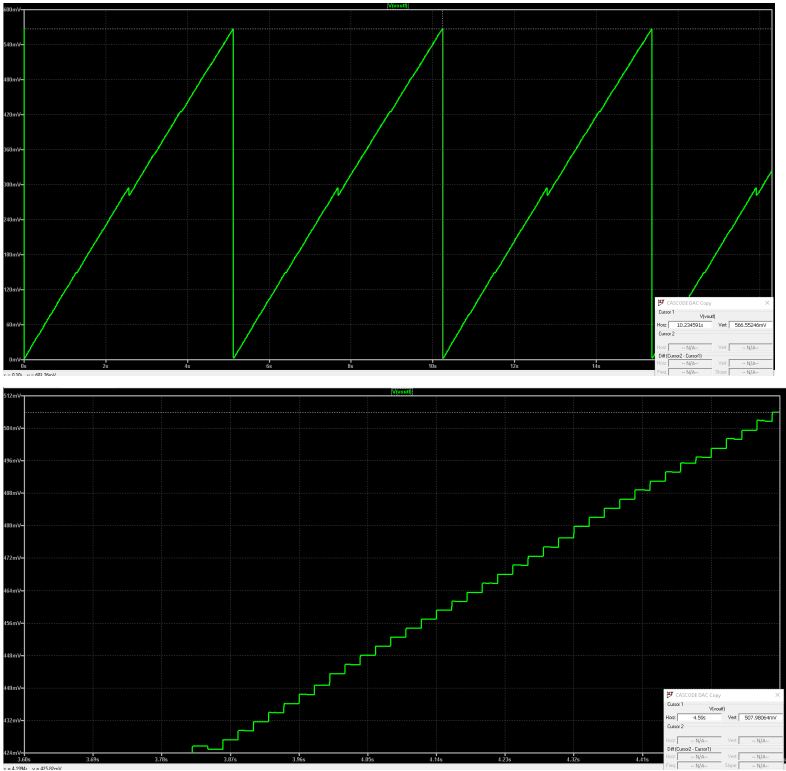


NOISE ANALYSIS

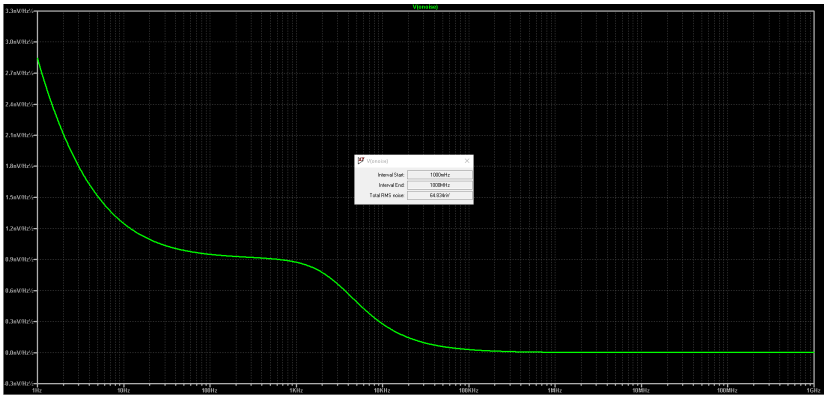

SOOCH CURRENT MIRROR DAC

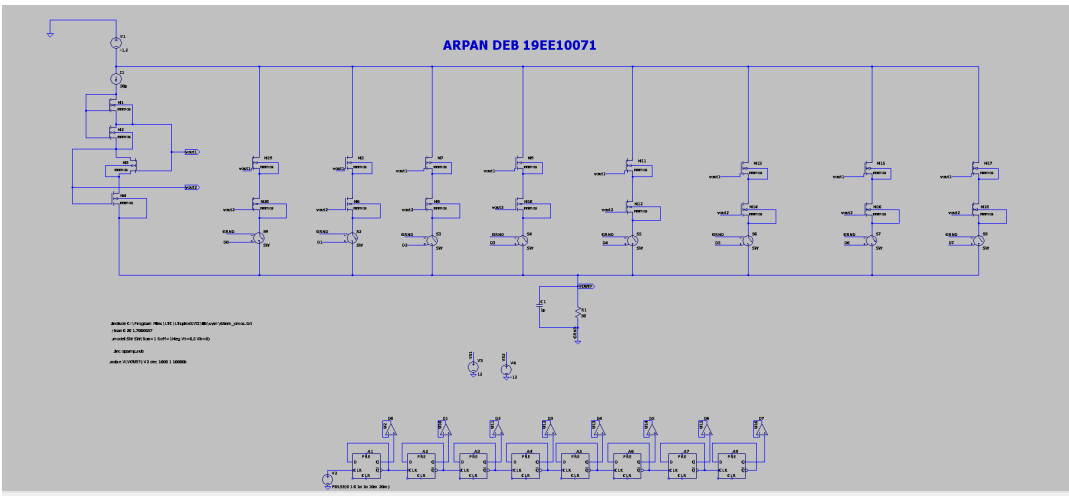

OUTPUT WAVEFORM

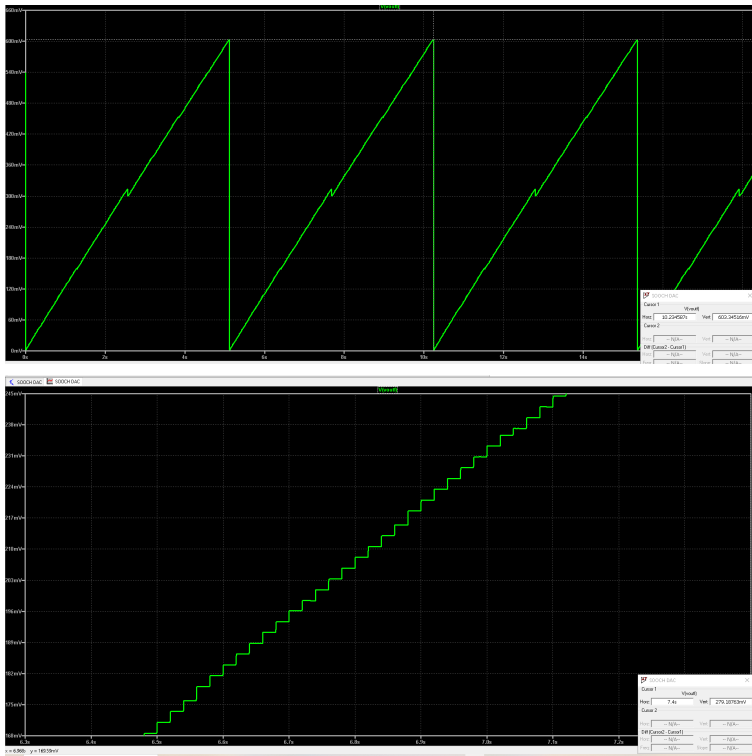

NOISE ANALYSIS

